
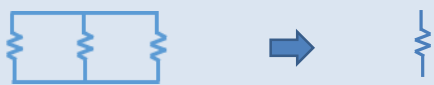


## CONCEPT: SOLVING RESISTOR CIRCUITS


- In Circuit problems, you will need to find the CURRENT and VOLTAGE of different Resistors.

SERIES CONNECTION	PARALLEL CONNECTION
<ul style="list-style-type: none"><li>- Equivalent Resistance: <math display="block">R_{eq} = R_1 + R_2 + R_3</math></li><li>- Share [ CURRENT / VOLTAGE ] with EACH OTHER</li><li>- Share [ CURRENT / VOLTAGE ] with EQUIVALENT Resistor</li></ul> 	<ul style="list-style-type: none"><li>- Equivalent Resistance: <math display="block">1/R_{eq} = 1/R_1 + 1/R_2 + 1/R_3</math></li><li>- Share [ CURRENT / VOLTAGE ] with EACH OTHER</li><li>- Share [ CURRENT / VOLTAGE ] with EQUIVALENT Resistor</li></ul> 

- STEPS for Solving Resistor Circuits:


- 1) “Collapse” down to ONE EQUIVALENT Resistor
- 2) Find VOLTAGE and CURRENT on Equivalent Resistor
- 3) “Work backwards” noting VOLTAGE and CURRENT on EACH Resistor

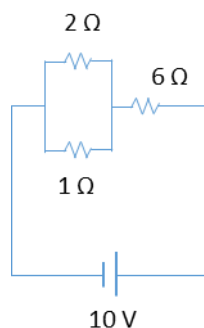EXAMPLE: What is the current and voltage of each of the resistors in the following circuit?



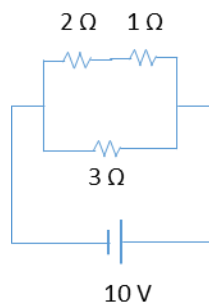
**PRACTICE: FIND CURRENT & VOLTAGE IN ALL RESISTORS**

What is current and voltage across each resistor below?



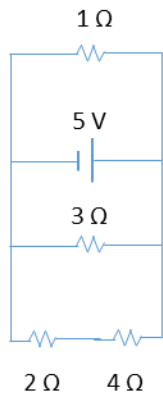**EXAMPLE: FIND CURRENT OF ONE CAPACITOR**

What is the current on the  $3\ \Omega$  resistor below?



**PRACTICE: FIND VOLTAGE OF THE BATTERY**

What is the voltage of the battery below?

