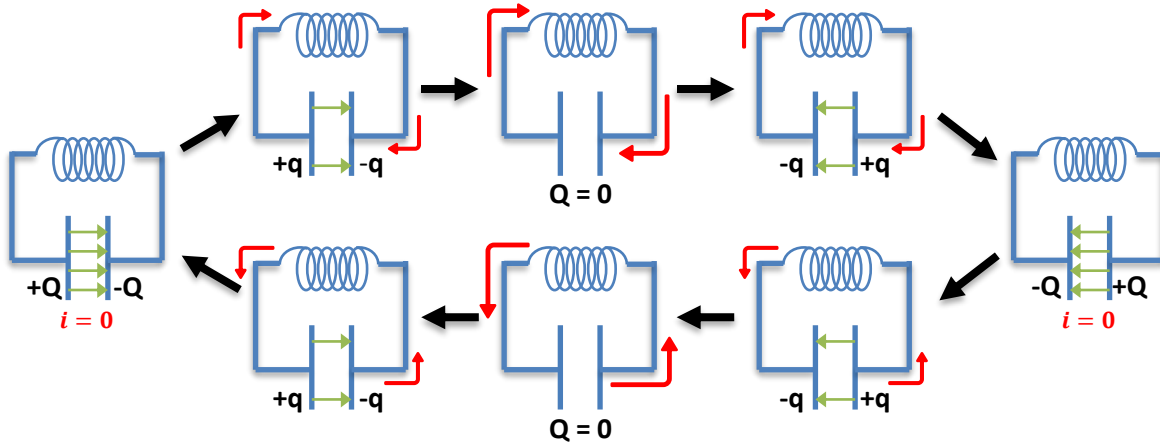


## CONCEPT: LC CIRCUITS

- LC Circuits are made up of \_\_\_\_\_ and \_\_\_\_\_ and follow an 8-step cycle.



- This system \_\_\_\_\_ and behaves similarly to **Simple Harmonic Motion** (Block + Spring)

- Because the system oscillates, the **charge** and **current** are represented by \_\_\_\_\_ functions.

-  $q(t) =$  \_\_\_\_\_

$\omega = \sqrt{\frac{1}{LC}}$  → angular frequency of oscillation

-  $i(t) =$  \_\_\_\_\_

$\phi$ : PHASE ANGLE → determines starting point of oscillation

- Note:** Make sure calculators are in RADIANS mode!

EXAMPLE: A capacitor with capacitance  $5 \times 10^{-9} \text{F}$  initially has charge of magnitude  $2 \times 10^{-4} \text{C}$  on each plate. The charged capacitor is then connected to an inductor with inductance  $4.0 \text{H}$ . During the current oscillations that occur after the circuit is completed, what is the maximum current in the inductor?

### **PRACTICE: PHASE ANGLE IN LC CIRCUIT**

An LC circuit with an inductor of  $0.05\text{ H}$  and a capacitor of  $35\text{ }\mu\text{F}$  begins with the current of  $-1\text{ A}$ . The capacitor plates have a maximum charge of  $2.65\text{ mC}$  at any time during the oscillation. What is the phase angle of this oscillation?

### **EXAMPLE: OSCILLATIONS IN AN LC CIRCUIT**

An LC circuit with  $L = 0.05\text{ H}$  and  $C = 50\text{ mF}$  begins with the capacitor fully charged. After  $0.1\text{ s}$ , the current is  $0.2\text{ A}$ . Under these conditions, how many seconds does it take for a fully charged plate to transfer all of its charge to the other plate?

## CONCEPT: ENERGY IN AN LC CIRCUIT


- Because there is no resistance, energy is conserved in an LC circuit:
  - Energy oscillates between \_\_\_\_\_ energy (Capacitor) and \_\_\_\_\_ energy (Inductor)

- A capacitor stores ELECTRICAL ENERGY

$$- U_C = \frac{1}{2} CV^2 = \frac{1}{2} QV = \frac{1}{2} \frac{Q^2}{C}$$

- An inductor stores MAGNETIC ENERGY

$$- U_L = \underline{\hspace{2cm}}$$

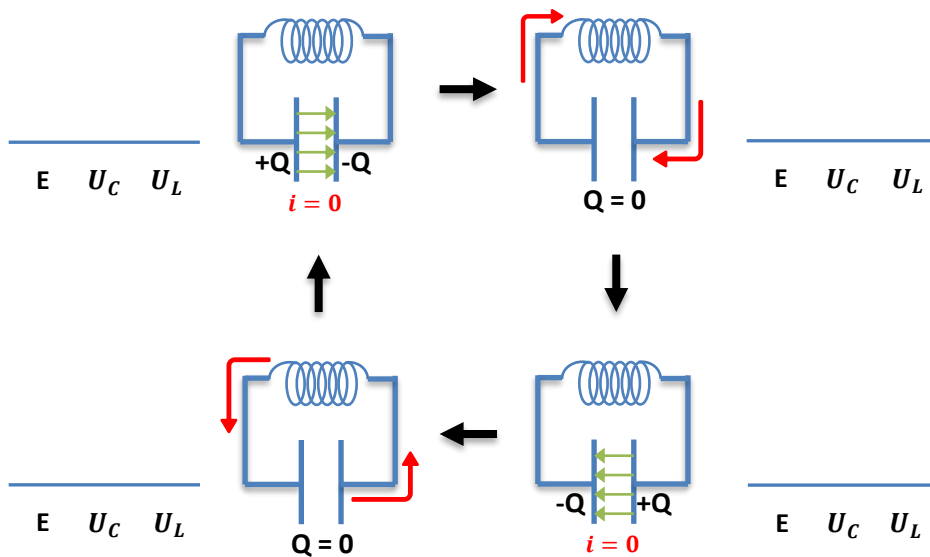

EXAMPLE: An LC circuit has an 0.1 H inductor and a 15 nF capacitor, and begins with the capacitor maximally charged with 50mC. After 0.1 s, **a)** how much energy is stored by the inductor? **b)** What is the maximum current in the circuit?

**PRACTICE: LC CIRCUIT WITH UNKNOWN INDUCTOR**

In an oscillating LC circuit in which the capacitance  $C = 4\mu\text{F}$  and the maximum voltage across the capacitor  $V = 1.50\text{V}$ , the maximum current measured across the inductor is  $50\text{mA}$ . What is the angular frequency of this LC circuit?