


CONCEPT: COMBINING CAPACITORS IN SERIES AND PARALLEL

- In Circuit problems, we can COLLAPSE / COMBINE capacitors into a SINGLE _____ capacitor.

SERIES CONNECTION	PARALLEL CONNECTION
<ul style="list-style-type: none">- Direct connection,- Equivalent Capacitance: $\frac{1}{C_{eq}} = \underline{\hspace{2cm}}$	<ul style="list-style-type: none">- Splits off, forms a loop- Equivalent Capacitance: $C_{eq} = \underline{\hspace{2cm}}$


- For circuits with combinations, find C_{eq} 's from inside \rightarrow outside.

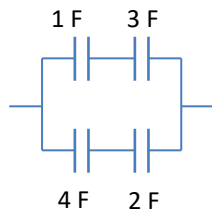EXAMPLE: What is the equivalent capacitance of the following capacitors?




- For TWO capacitors in SERIES, $C_{eq} = \underline{\hspace{2cm}}$

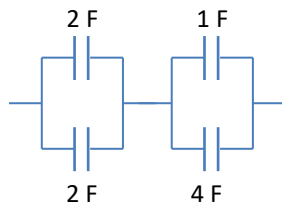EXAMPLE: What is the equivalent capacitance of the following capacitors?



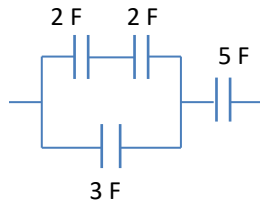EXAMPLE: EQUIVALENT CAPACITANCE OF 4 CAPACITORS

What is the equivalent capacitance of the following combination of capacitors?



PRACTICE: EQUIVALENT CAPACITANCE OF 4 CAPACITORS

What is the equivalent capacitance of the following capacitors?

