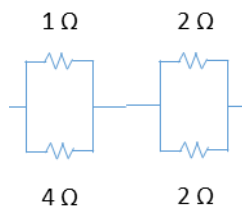


## CONCEPT: COMBINING RESISTORS IN SERIES AND PARALLEL


- In Circuit problems, you will need to COLLAPSE / COMBINE resistors into a SINGLE \_\_\_\_\_ resistors.

SERIES CONNECTION	PARALLEL CONNECTION
<ul style="list-style-type: none"><li>- Direct connection, no splits</li><li>- Equivalent Resistance <math>\rightarrow R_{eq} = \underline{\hspace{2cm}}</math></li><li>- Always _____ than individual resistances</li></ul>	<ul style="list-style-type: none"><li>- Wire splits, forms a loop</li><li>- Equivalent Resistance <math>\rightarrow R_{eq} = \underline{\hspace{2cm}}</math></li><li>- Always _____ than individual resistances</li></ul>

EXAMPLE 1: What is the equivalent resistance of the following resistors?




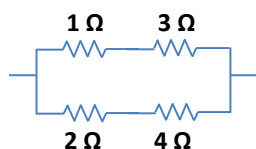EXAMPLE 2: What is the equivalent resistance of the following resistors?



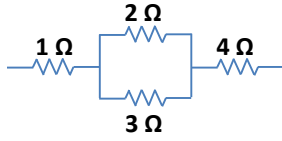**PRACTICE: EQUIVALENT RESISTANCE #1**

What is the equivalent resistance of the following combination of resistors?




### CONCEPT: SHORTCUT EQUATIONS FOR RESISTORS IN PARALLEL

- SHORTCUT #1: If you have TWO resistors in Parallel, you can use:

→ Note this does NOT work if you have more than 2 resistors!


- SHORTCUT #2: If you have resistors of SAME resistance in Parallel, you can use:

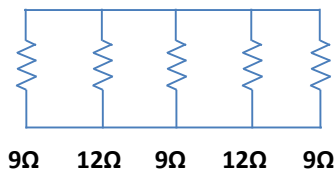EXAMPLE: What is the equivalent resistance of the following network of resistors?



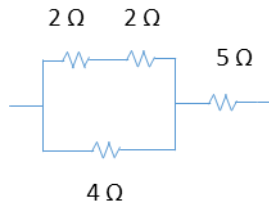
### PRACTICE: EQUIVALENT RESISTANCE #2

What is the equivalent resistance of the following combination of resistors?


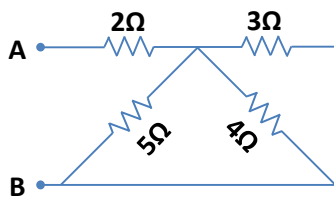
### EXAMPLE: EQUIVALENT RESISTANCE OF WEIRD ARRANGEMENT

What is the equivalent resistance of the following resistors?



**PRACTICE: EQUIVALENT RESISTANCE WITH VARIABLES**

If every resistor below has resistance  $R$ , what is the equivalent resistance of the combination, in terms of  $R$ ?

